

CALIFORNIA STATE UNIVERSITY, BAKERSFIELD (CSUB)

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING & COMPUTER SCIENCE

ECE 3320: FIELDS AND WAVES

Laboratory 3

First, get familiar with the oscilloscope. It is a powerful tool for looking at waveforms. This allows voltages to be measured as a function of time.

1. Measure the voltage from the power supply. You should see a fairly constant line.
2. Now, connect the function generator to the oscilloscope. Make a 1kHz sine wave with the function generator. Measure the period of the sine wave (the time from peak to peak). Calculate the frequency from the period. Measure the amplitude.
3. Try changing the amplitude and frequency of the waveform. Change the waveform from sine to triangle. Change from triangle to square. For the different waveforms, find the amplitude and frequency.

Make sure to take pictures of the plots and oscilloscope screen. To take pictures of the oscilloscope screen, insert a flash drive into the USB port. Then, click Save/Recall -> Change Print Button to Save All to Files. You can select the folder and also change action to save image under different format. Then click the print button to save. The second way to take pictures of the oscilloscope is to use the OpenChoice Desktop software on the computer. The oscilloscope needs to be on before you turn on the computer.

The basic equation for capacitors is $Q=CV$, where Q is the charge, C is the capacitance, and V is the voltage. Make sure the orientation of the capacitor is correct. The negative side of the capacitor has a shorter lead and sometimes an arrow pointing to it.

For Parts A, B, D, and E, you will be finding the value of the two small capacitors (blue/purple one and black one). First, do the part for the first small capacitor. Then, repeat the part with the other small capacitor replacing the first small capacitor. For Part C, you will be using the big capacitor.

A. Finding the capacitance in parallel

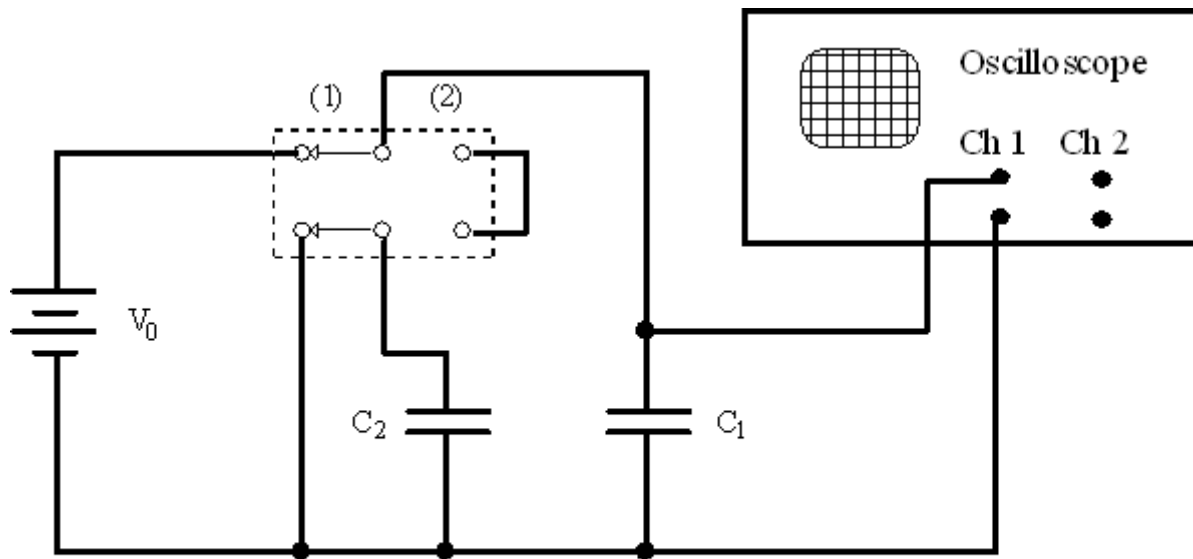


Figure 1. Setup for parallel capacitors test..

Set up the circuit in Figure 1. From Figure 1, we have two capacitors. Capacitor 1 (C_1) is unknown and capacitor 2 (C_2) is a decade capacitance box. Use $1\mu\text{F}$, $2\mu\text{F}$, $3\mu\text{F}$, and $4\mu\text{F}$ on the decade capacitance box as four different values of C_2 . For parallel capacitors, $C_{eq}=C_1+C_2$. When the switch is in position 1, capacitor 1 can be described by the following equation. $Q_1=C_1*V_0$ while capacitor 2 is discharged. After the switch goes to position 2, the total charge $Q=Q_1+Q_2$. But, $Q_2=0$ since it is discharged. Therefore $Q=Q_1$. This becomes $C_{eq}V=C_1*V_0$. Plugging in for C_{eq} gives $(C_1+C_2)*V=C_1*V_0$. This gives $V=V_0*C_1/(C_1+C_2)$. Rearranging the equation becomes $V_0/V=C_2/C_1+1$. The value of C_2 can change. As C_2 changes, V can also change according to the equations.

1. With the DPDT knife switch, make sure all 6 wires are touching each metal part and are not loose. Keep the switch in position 1. C_2 is discharged while C_1 is charged to V_0 . Try using a V_0 of 15V from the power supply. Read the voltage on the oscilloscope. On the oscilloscope, use 5V/div and 500ms/div. Move the switch to position 2. C_1 and C_2 are in parallel. Right after you move the switch, the voltage should have a sudden drop. Read the voltage across the capacitors in parallel on the oscilloscope right after it drops. After some time, the voltage will quickly drop to zero. Hit "Run/Stop" on the oscilloscope to stop the screen from changing. Then, use "Cursor" on the oscilloscope to read the voltage.
2. Repeat the measurement several times to make sure it is correct. Also, repeat for different values of C_2 .
3. Make a plot of V_0/V vs C_2 . Find the value of C_1 from the plot. To do this in LibreOffice Calc, enter the x values in one column. Enter the y values in the next column. Highlight the x and y

values. Then, insert chart from the top menu by going to “Insert” -> “Object” -> “Chart”. For chart type, choose XY (Scatter). Click on points in the chart. Then go to “Insert” -> “Trend Lines” -> Select “Linear” and Check “Show Equation”. For this part, C_2 are the x values and V_0/V are the y values. Then, the slope is equal to $1/C_1$.

4. Find the unknown capacitance of both small capacitors. There is a blue/purple small capacitor and a black small capacitor

B. Finding the capacitance in series

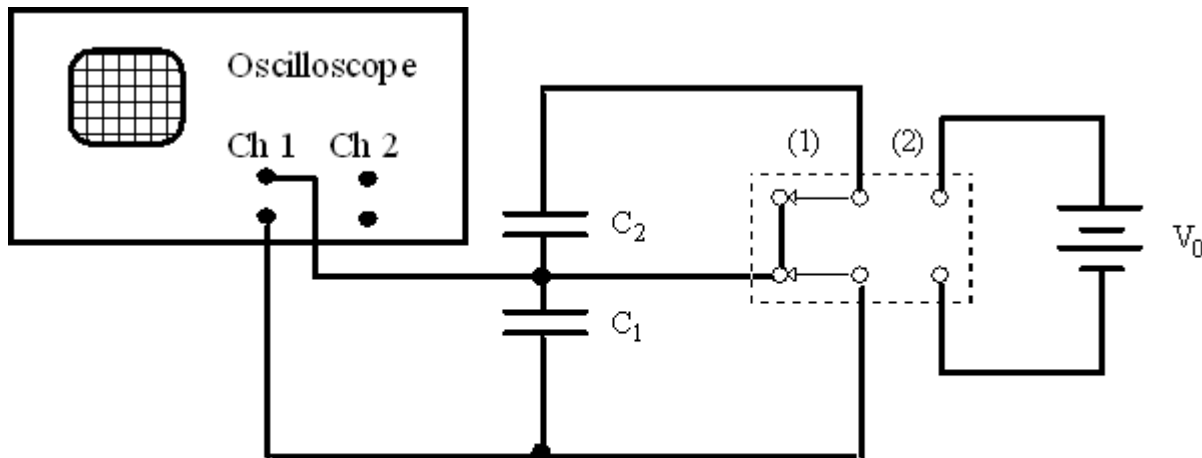


Figure 2. Setup for series capacitor test..

Set up the circuit in Figure 2. The two capacitors are not charged in position 1. Capacitor 1 (C_1) is unknown and capacitor 2 (C_2) is a decade capacitance box. Use $1\mu\text{F}$, $2\mu\text{F}$, $3\mu\text{F}$, and $4\mu\text{F}$ on the decade capacitance box as four different values of C_2 . On position 1, the voltage should be zero across the capacitors since the capacitors are discharged. When switched to position 2, you should see a sudden jump in voltage. When switched to position 2, record the voltage V_1 across C_1 right after it jumps. After recording the voltage, flip the switch back to position 1. Repeat several times. Do the same for voltage V_2 across C_2 right after it jumps. For each C_2 , V_1 and V_2 should add up to V_0 (about 15V). Repeat for different values of C_2 . You cannot use two probes to measure V_1 and V_2 at the same time. You have to use one probe to measure V_1 and then use one probe to measure V_2 .

For capacitors in series, $C_{eq} = C_1 C_2 / (C_1 + C_2)$, $Q_1 = Q_2 = Q$, and $V_0 = V_1 + V_2$.

$$Q = C_{eq} (V_1 + V_2)$$

$$C_1 V_1 = C_{eq} V_0$$

$$C_1 V_1 = (C_1 C_2) V_0 / (C_1 + C_2)$$

$$V_1 = C_2 V_0 / (C_1 + C_2)$$

$$V_2 = C_1 V_0 / (C_1 + C_2)$$


After measuring voltages V_1 and V_2 , find the unknown capacitance. Rearranging the last two equations will give you the equation for the unknown capacitor. You should get similar values for C_1 from both equations. Use the same two capacitors before in part A and find both unknown capacitance again.

$$C_1 = (C_2 V_0 - V_1 C_2) / V_1$$


$$C1 = V2 * C2 / (V0 - V2)$$

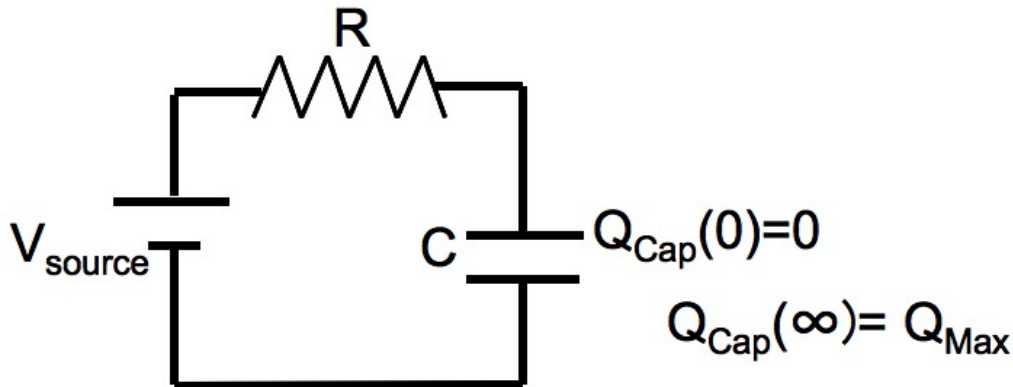C. Finding the capacitance in a RC circuit with DC source

So far, no resistor was used, so the discharge from the capacitors was fairly quick. Set up the following circuit. Use the biggest capacitor. At first, the capacitor has a constant voltage across it from the dc source.




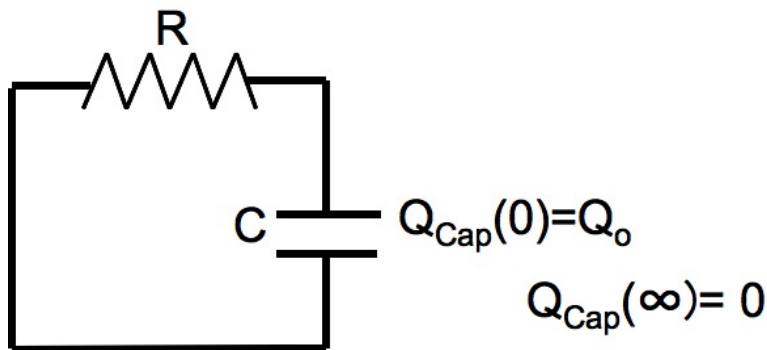Disconnect the voltage source and discharge the capacitor. If you have a resistor, the time dependent equation for the voltage across a discharging capacitor is $V_{\text{Cap}}(t) = V_0 e^{-\frac{t}{RC}}$. Remember in MATLAB, there is log and log10 commands. We are using a 10000 ohm resistor. Observe the voltage across the capacitor. Use 1sec/div.



1. Try using an initial voltage of 15V. Check your highest voltage value with the oscilloscope. It may not have reached 15V. The highest voltage value before it starts decreasing will be your initial voltage V_0 . Measure the time it takes to discharge to 80%, 60%,... of the initial voltage.
2. To do step 1, use two cursors. Put one cursor at the beginning when the voltage starts to drop. Move the second cursor around. Read the voltage on the second cursor and Δt .
3. Do the above ten times.
4. Average the results.
5. Plot $[-\ln(V/V_0)]$ against time.
6. Draw a straight line. From the slope get the value of C. The slope should be equal to $1/(R * C)$.

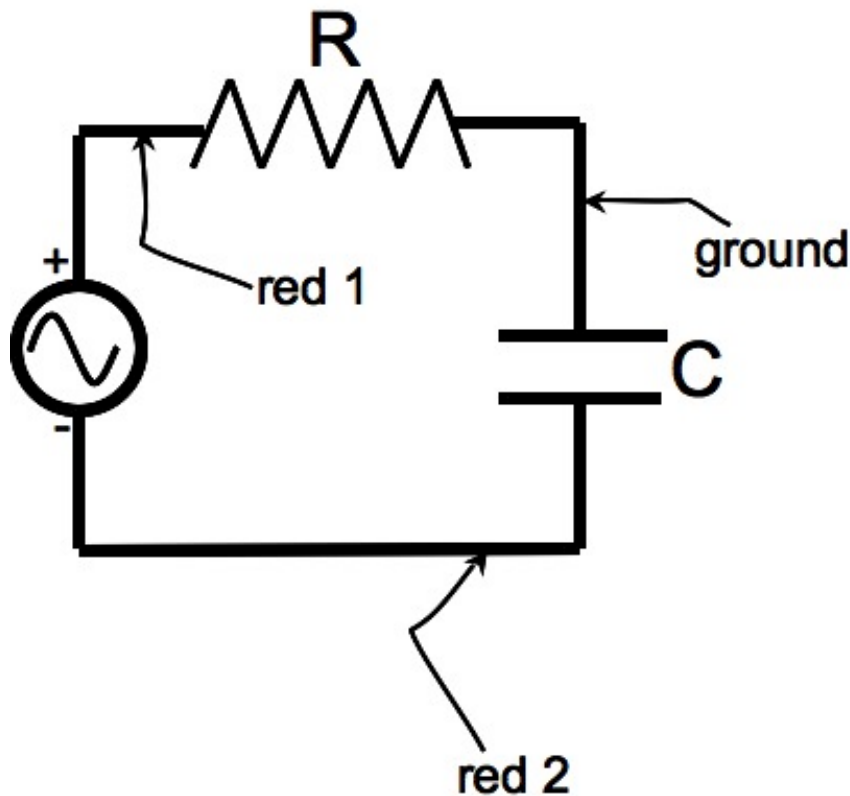D. Finding the capacitance in a RC circuit with AC source (1st method)



What happens if we use an AC source instead of a DC source? Set your function generator to create a sine wave voltage that has a peak-to-peak amplitude of a nice round number like 3V. You may want to adjust your frequency later, but start at about 1 Hz. Use a resistor of around 10000 ohms.

Next you will test the relationship $X_C = \frac{1}{\omega_D C}$ by observing a sinusoidally driven RC circuit using many different driving frequencies. As you increase the driving frequency, the amplitude of the resistor voltage will increase because the total circuit impedance is decreasing, i.e. $V_{\text{resistor amplitude}} = \frac{R}{Z} V_{\text{source amplitude}}$.

Meanwhile, as the driving frequency increases, the capacitor amplitude decreases. This makes sense because the resistor and the capacitor are the only two components in the circuit other than the source. Since the voltages across both must add up to the source voltage at any instant in time, if the voltage amplitude of one increases, then the other must decrease.

Therefore, there must be some specific driving frequency when the amplitude of the resistor voltage matches the capacitor voltage: $V_{\text{resistor amplitude}} = V_{\text{capacitor amplitude}}$ for a specific angular driving frequency $\omega_{D,\text{match}}$.

Realizing that $V_{\text{resistor amplitude}} = \frac{R}{Z} V_{\text{source amplitude}}$ and $V_{\text{capacitor amplitude}} = \frac{X_C}{Z} V_{\text{source amplitude}}$, setting these two voltages equal when at the matching angular driving frequency $\omega_{D,\text{match}}$ you get $\frac{X_C}{Z} V_{\text{source amplitude}} = \frac{R}{Z} V_{\text{source amplitude}}$, which simplifies to

$X_C = R$. In other words, the voltage across the capacitor equals the voltage across the resistor if their "resistances" are equal, which kind of makes sense.

The “single measurement” method for finding the capacitance of an unknown capacitor makes use of the previous equation, $X_C = R$. All you need to do is adjust the driving frequency of your circuit until the capacitor voltage amplitude and the resistor voltage amplitude are equal. Then use $X_C = R$

(substituting $X_C = \frac{1}{\omega_{D,match} C}$) for the specific $\omega_{D,match}$ to find the capacitance.

1. You do not need to measure with the probes across the resistor. Only use the probes to measure across the capacitor and across the total voltage with the oscilloscope. Do not set up middle ground like in the figure or you cannot measure the voltage across the capacitor. Connect the function generator and capacitor to the same ground.
2. Use the “Math” button to get subtraction and (Ch1-Ch2). Ch1 is the total voltage. Ch2 is the voltage across the capacitor. The Math waveform is the voltage across the resistor. Use 1V/div for Ch1, Ch2, and Math. You may need to adjust the time scale.
3. Use “Measure” on the oscilloscope to find the peak-to-peak voltage of the capacitor and the peak-to-peak voltage of the resistor. If it is not giving a value, go to Trig Menu and change the mode from Auto to Normal or try hitting Autoset.
4. Starting from 1 Hz, adjust the frequency until the peak-to-peak voltage of the capacitor is equal to the peak-to-peak voltage of the resistor. Enter this frequency and $X_C = R = 10000$ ohms into the equation $C = \frac{1}{2 * \pi * f * X_C}$
5. Do this for both small capacitors.

E. Finding the capacitance in a RC circuit with AC source (2nd method)

The “multiple measurements” method for finding an unknown capacitance is more involved, but more accurate as it involves multiple measurements. The voltage amplitudes of the sinusoidally driven RC are:

$$V_{\text{resistor amplitude}} = \frac{R}{Z} V_{\text{source amplitude}}$$

and

$$V_{\text{capacitor amplitude}} = \frac{X_C}{Z} V_{\text{source amplitude}}.$$

Dividing these two equations gives

$$\frac{V_{\text{capacitor amplitude}}}{V_{\text{resistor amplitude}}} = \frac{\left(\frac{X_C \cdot V_{\text{source amplitude}}}{Z} \right)}{\left(\frac{R \cdot V_{\text{source amplitude}}}{Z} \right)} = \frac{X_C}{R}$$

Therefore,

$$X_C = R \frac{V_{\text{capacitor amplitude}}}{V_{\text{resistor amplitude}}}$$

In order to experimentally determine C for your capacitor, simply combine the last equation with the definition $X_C = \frac{1}{\omega_{\text{drive}} C}$ and rearrange:

$$\frac{1}{R} \frac{V_{\text{resistor amplitude}}}{V_{\text{capacitor amplitude}}} = C \omega_D$$

$$\frac{1}{R} \frac{V_{\text{resistor amplitude}}}{V_{\text{capacitor amplitude}}} = C \omega_D$$

looks like a weird arrangement for this equation, but if you think of $y=mx$, then you see that if you

graph $\frac{1}{R} \frac{V_{\text{resistor amplitude}}}{V_{\text{capacitor amplitude}}}$ vs. ω_D , you should obtain a linear graph with a slope equal to C.

1. Like in part D, use the probes to measure the peak-to-peak voltage of the capacitor on the oscilloscope for different frequencies. Also, measure with probes across the total voltage on the oscilloscope.
2. Use the “Math” button to get subtraction and (Ch1-Ch2). Ch1 is the total voltage. Ch2 is the voltage across the capacitor. The Math waveform is the voltage across the resistor.
3. Use “Measure” on the oscilloscope to find the peak-to-peak voltage of the capacitor and the peak-to-peak voltage of the resistor. If it is not giving a value, go to Trig Menu and change the mode from Auto to Normal or try hitting Autoset or wait a

while for the screen to change.

4. Make a plot of $\frac{1}{R} \frac{V_{\text{resistor amplitude}}}{V_{\text{capacitor amplitude}}}$ vs. ω_D . ω_D is equal to $2\pi \times \text{frequency}$. R is still 10000

ohms

5. Do this for both small capacitors.

F. Finding the capacitance from the physical characteristics

The capacitance can also be found by the equation

$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$

where A is the area of overlap of the two plates; ϵ_r is the relative static permittivity, ϵ_0 is the electric constant ($\epsilon_0 \approx 8.854 \times 10^{-12} \text{ F m}^{-1}$); and d is the separation between the plates.